

Contents

<i>Preface</i>	vi
<i>Acknowledgements</i>	vii
1. The Common Cathode, Triode Gain Stage	1
Fundamentals of amplification	1
The load line	3
Biasing and distortion	4
Grid-current limiting	7
Cut-off	9
Headroom: input sensitivity and the threshold of clipping	10
Limitations on bias	12
Applying bias	14
Fixed bias	14
Cathode bias	14
Grid-leak bias	15
Designing a simple, triode gain stage	15
Choosing the anode load resistor	15
Choosing the cathode bias resistor	17
The cathode load line	18
Choosing the grid-leak resistor	19
Calculating power ratings	20
The valve constants	21
Transconductance	21
Amplification factor	22
Anode resistance	22
Mathematical treatment of a gain stage	23
The cathode bypass capacitor	25
Other cathode bypass circuits	28
Input and output impedance	31
The Miller effect	32
Cathode biasing with diodes	34
Summary of formulae	36
2. Coupling	38
The amplifier's input	38
The input grid-stopper	39
Fundamentals of interstage AC coupling	41
The AC load line	43
Blocking distortion and grid stoppers	46
Practical AC coupling networks	48
Wide-band attenuation	48
Treble boost (bass cut) and 'bright' capacitors	50
Treble cut (bass boost) and anode bypass capacitors	54
DC coupling	57
Direct coupling	57
Level shifting	60
Summary of formulae	64

3. The Small-Signal Pentode	66
The suppressor grid (g3)	66
The screen grid (g2)	67
The effect of screen voltage	68
The effect of screen current	70
Pentodes connected as triodes	72
Noise in pentodes	73
Designing pentode gain stages	75
Choosing the anode resistor	75
Choosing the screen voltage	77
Adapting the anode characteristics for any screen voltage	81
Choosing the cathode bias resistor	82
Designing the screen-supply circuit	84
Mathematical treatment of the pentode gain stage	87
Gain	87
The effect of screen bypassing	87
The effect of cathode bypassing	90
Output impedance	92
Input capacitance	92
Switchable and variable pentode designs	92
Triode/pentode switches	93
Variable screen bypassing	94
Triode/pentode ‘morph’ control	95
Summary of formulae	97
4. Valves in Parallel	100
The Matchless input stage	103
The common-anode mixer	105
Switchable designs	109
5. The Cathode Follower	113
Fundamental parameters of the cathode follower	113
Gain	113
Input capacitance	114
Input impedance	114
Output impedance	114
Graphical analysis	115
Biasing arrangements for AC-coupled cathode followers	118
Fixed bias	118
Cathode bias	119
DC-coupled cathode followers	122
The pentode as a cathode follower	125
Cathode followers in guitar amps	126
Bootstrapping for more gain	131
Summary of formulae	135

6. The Cascode	137
Basic operation of the cascode	137
The effect of the ‘screen grid’ voltage	138
Deriving anode-characteristics graphs	140
Fundamental parameters of the cascode	143
Gain	143
Input capacitance	143
Output impedance	144
Designing a cascode	144
Applying fixed bias to the upper triode	147
Choosing the cathode bypass capacitor	148
Applying cathode bias to the upper triode	150
Applying grid-leak bias to the upper triode	152
Current-boosted cascodes	154
Summary of formulae	157
7. The Cathodyne Phase Inverter	159
Fundamental parameters of the cathodyne phase inverter	160
Gain	160
Input capacitance	161
Input impedance	161
Output impedance	161
Output bandwidth	162
Designing a cathodyne	163
Biasing arrangements for AC-coupled cathodynes	165
Fixed bias	165
Cathode bias	166
DC-coupled cathodynes	168
Overload characteristics of the cathodyne	169
The ‘gain-spike’ effect	169
The frequency-doubling effect	170
Avoiding unpleasant distortion effects	172
Bootstrapping for gain	173
Summary of formulae	174
8. The Long-Tailed Pair Phase Inverter	176
Basic operation of the long-tailed pair	176
Fundamental parameters of the long-tailed pair	177
Input capacitance	179
Input impedance	179
Output impedance	179
Input sensitivity	180
Designing a long-tailed pair	180
DC-coupled long-tailed pairs	182
AC-coupled long-tailed pairs	184
Fixed bias	184
Cathode bias	185

Global negative feedback and the long-tailed pair	187
A worked example; the Fender <i>5F6-A Twin Amp</i>	189
The presence control	192
Variable feedback	194
Presence control without global negative feedback	195
‘Scale’ control	196
Overload characteristics of the long-tailed pair	197
Summary of formulae	199
9. Feedback Theory	201
The universal feedback equation	201
Practical, local-feedback amplifiers	203
Effect on linearity, noise and frequency response	204
Effect on input and output impedance	206
Practical, virtual-earth amplifiers	208
Effects on overdrive	210
Stability and limitations on feedback	211
Stabilising a feedback amplifier	214
Global feedback in practice	218
Choosing the feedback resistor	222
Summary of formulae	227
10. Tone controls and tone stack	229
Notes on impedance bridging	230
Notes on design	230
Basic, ‘one knob’ tone controls	230
Treble	231
Bass	233
Middle	235
Tilt control	236
Tone stacks	238
The Bandmaster tone stack	238
The Voigt tone stack	239
The James tone stack	240
The passive Baxandall tone stack	241
The FMV tone stack	242
Designing an FMV tone stack	243
Expanding the MFV tone stack	247
Ultra-low switch	247
Defeat / lift	248
Shift control	249
11. Effects Loops	251
Line levels	253
Send, line out and loop drivers	254
Simple line-out arrangements	254
Active loop drivers	259
Recovery stages and serial effects loops	263

Passive serial loops	264
Active serial loops	266
Parallel effects loops	268
Passive parallel loops	268
Active parallel loops	270
12. Notes on Construction	275
Grounding	275
The earth bond	275
Ground loops	277
Bus grounding	278
Star grounding	279
The power supply	281
The heater supply	284
Heater lead dress	284
Hum balance	286
Heater elevation	287
A note on lead dress	288
<i>Bibliography</i>	289
<i>Index</i>	292